SMART FARMER IOT ENABLED SMART FARMING APPLICATION

ASSIGNMENT-01

SUBMITTED BY

SHAMINI P (113219041105)

BACHELOR OF ENGINEERING IN ELECTRONICS AND COMMUNICATION ENGINEERING

Make a Smart Home in Tinkercad using 2+ sensors, LED, buzzer in single code and circuit.

Source code:

```
int t=2;
int e=3;
void setup() {
Serial.begin(9600);
pinMode(t,OUTPUT);
pinMode(e,INPUT);
pinMode(12,OUTPUT);
} void loop() {
digitalWrite(t,LOW);
digitalWrite(t,HIGH);
delayMicroseconds(10);
digitalWrite(t,LOW);
float dur=pulseIn(e,HIGH);
float dis=(dur*0.0343)/2;
Serial.print("Distance is: ");
Serial.println(dis);
if(dis>=100) {
```

```
digitalWrite(8,HIGH);
digitalWrite(7,HIGH);
if(dis >= 100)
for(int i=0; i<=30000; i=i+10)
tone(12,i);
delay(1000);
noTone(12);
delay(1000);
double a= analogRead(A0);
double t = (((a/1024)*5)-0.5)*100;
Serial.print("Temp Value: "); S
Serial.println(t);
delay(1000);
if(t>=100) {
digitalWrite(8,HIGH);
digitalWrite(7,HIGH);
if(t>=100)
for(int i=0; i<=30000; i=i+10)
tone(12,i);
delay(1000);
noTone(12);
```

```
delay(1000);
}

if(t<100)
{
digitalWrite(8,LOW);
digitalWrite(7,LOW);
}</pre>
```

CIRCUIT DIAGRAM:

