

**SMART FARMER IOT ENABLED SMART
FARMING APPLICATION**

ASSIGNMENT-01

SUBMITTED BY

LEELA VINOTHINI S (113219041056)

**BACHELOR OF ENGINEERING IN
ELECTRONICS AND
COMMUNICATION ENGINEERING**

—

Make a Smart Home in Tinkercad using 2+ sensors, LED, buzzer in single code and circuit.

Source code:

```
int t=2;
int e=3;

void setup() {
  Serial.begin(9600);
  pinMode(t,OUTPUT);
  pinMode(e,INPUT);
  pinMode(12,OUTPUT);
} void loop() {
  digitalWrite(t,LOW);
  digitalWrite(t,HIGH);
  delayMicroseconds(10);
  digitalWrite(t,LOW);
  float dur=pulseIn(e,HIGH);
  float dis=(dur*0.0343)/2;
  Serial.print("Distance is: ");
  Serial.println(dis);
  if(dis>=100) {
```

```
digitalWrite(8,HIGH);
digitalWrite(7,HIGH);
}
if(dis>=100)
{
for(int i=0; i<=30000; i=i+10)
{
tone(12,i);
delay(1000);
noTone(12);
delay(1000);
}
}
double a= analogRead(A0);
double t=((a/1024)*5)-0.5)*100;
Serial.print("Temp Value: "); S
Serial.println(t);
delay(1000);
if(t>=100) {
digitalWrite(8,HIGH);
digitalWrite(7,HIGH);
}
if(t>=100)
{
for(int i=0; i<=30000; i=i+10)
{
tone(12,i);
delay(1000);
noTone(12);
```

```
delay(1000);  
}  
}  
if(t<100)  
{  
digitalWrite(8,LOW);  
digitalWrite(7,LOW);  
}  
}
```

CIRCUIT DIAGRAM:

